

OPAMP DESIGN PROJECT

EE3002


Dhruvjyoti Bagadthey
EE17B156

AIM:

The aim of this project is to design an op amp using MOSFETS for gain 2 Amplifier operation having:


1. Closed Loop 3db Bandwidth of 5MHz
2. Phase margin > 60 degrees
3. Capacitive load = 10pf
4. Resistive load = 2.5k Ω

Circuit Diagram:

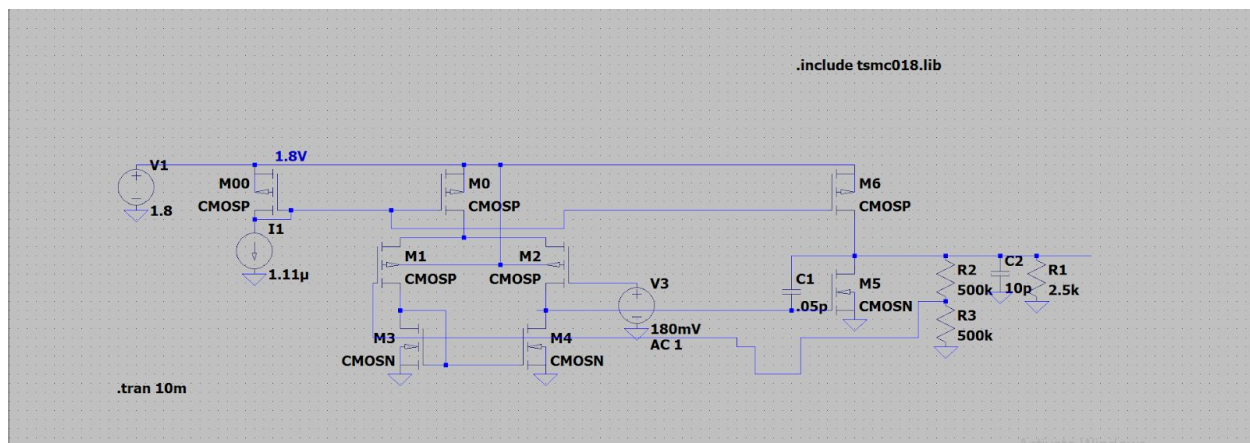

Above is the circuit diagram at closed loop operation.

Hand Calculations:

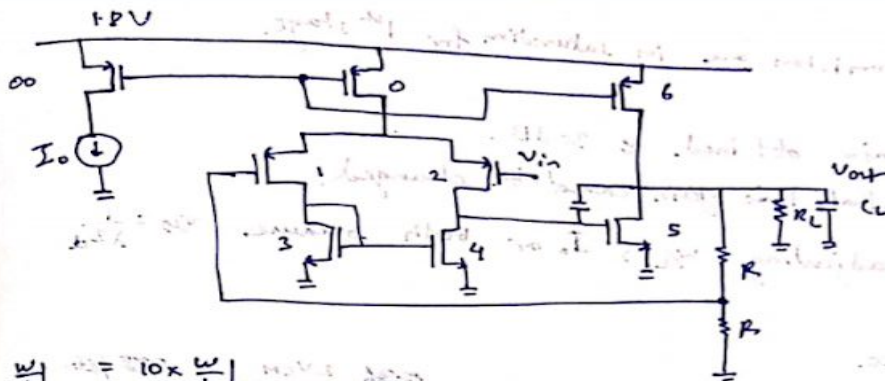

$$\frac{W}{L}_0 = 10 \times \frac{W}{L}_{op}$$

Initially; gate overdrive Voltage $\approx 200\text{mV} \Rightarrow V_{GS} - V_{TH} = 0.2$

$$V_{S3} = 0.57\text{V}$$

$$\therefore V_{CH} \approx 0.18\text{V}$$

However, if V_{CH} is too high $V_{out\ DC} = 2 \times V_{CH}$ will be high

$\therefore R_L = 2.5\text{k}\Omega$, a high current must flow through M_6

\therefore high $\frac{W}{L}$ for M_6

\therefore We keep $V_{CH} = 0.18\text{V}$ & decrease gate overdrive Voltage

$$\text{Let } V_{S3} = 0.54\text{V}$$

\therefore if we keep L v. small, small channel effects increase & V_{ds} decreases, we shall keep $L = 1.8\mu$ for proper current mirroring.

~~Simplest case;~~

$$\text{Simplest case; } \frac{W}{L}_0 = 1 \Rightarrow W_0 = 1.8\mu$$

$$\frac{W}{L}_1 = 10 \Rightarrow W = 18\mu$$

$$\frac{W}{L}_1 = \frac{W}{L}_2 = 5 \Rightarrow W = 9\mu$$

$$\frac{W}{L}_3 = \frac{W}{L}_4 = 5 \times \frac{10}{23} = 2.174\mu$$

$$\therefore I_{D3} = 4.5\mu\text{A} \Rightarrow I_0 = 0.9\mu\text{A}, \text{ but for } V_{S3} = 0.54\text{V},$$

The simulation requires pairing of $1.11\mu\text{A}$ & $I_{D3} = 5\mu\text{A}$
1, 2, 3, 4 are in saturation.

$$5\mu = \frac{1}{2} \times 100 \times 5 \times (V_{S3} - V_{TH})^2$$

$$\Rightarrow V_{D0} = 711\text{mV}$$

$$V_{S0} = 1.268\text{V} \therefore V_{D0} < V_{S0} \Rightarrow (\text{saturation})$$

\therefore all transistors are in saturation for 1st stage.

1st stage gain obtained $\approx 30\text{dB}$.

It is seen that this gain cannot be changed by merely adjusting W/L , I_0 or both because $V_{DS} = \frac{1}{\lambda I_D}$

Assume $R = \infty$.

\therefore for V_{CM} input; current through $R_1 = \frac{2V_{CM}}{R_1} = \frac{2 \times 0.7}{1000} = 144 \mu\text{A}$

for M5;

$$V_G = 0.54 \text{ V}$$

$$V_D = 0.36 \text{ V}$$

$$\therefore V_D \approx V_G - V_{Th} = 0.17 \text{ V} \Rightarrow \text{saturation}$$

current through M5 depends on $(W/L)_5$

Miller zero of Open loop Transfer functions lies @ $\frac{g_{m2}}{C} = \frac{g_{m5}}{C}$

While ~~dominant pole~~ Unity gain frequency Open loop TF lies @ $\frac{g_{m1}}{C} = \frac{g_{m1}}{C}$

$$\therefore g_{m2} \gg g_{m1}, \text{ let } g_{m2} = 10 g_{m1} \Rightarrow \left(\frac{W}{L}\right)_5 = 10 \left(\frac{W}{L}\right)_4$$

(AP) DC gain = $g_{m1} R_{O1} \times g_{m5} (R_{O2} \parallel R_L) \times \frac{1}{2}$

$$\omega_d = \frac{1}{g_{m5} R_{O2} C R_{O1}}$$

$$\omega_2 = \frac{g_{m5}}{C}$$

$$\omega_0 = \frac{g_{m1}}{C} \text{ for A; for AP; } \omega_0 = \frac{g_{m1}}{2C}$$

Let $C = 1\text{pF}$ & $\left(\frac{W}{L}\right)_6 = (200\text{n} : 1.8\mu)$

But in this case Open loop gain is $\approx 32\text{dB}$, it is smaller than the specification. \therefore we increase $\left(\frac{W}{L}\right)_5 = 100 \left(\frac{W}{L}\right)_4$

$$\therefore W_5 = 217.4 \mu\text{m}$$

$$L_5 = 1.8 \mu\text{m}$$

To match the current through $M6$ to currents through $M5$ & R_L @ $V_{O_{crp}} = 0.36V$; a parametric sweep was performed for W_6 keeping $L_6 = 1.0 \mu$, this value turned out to be $W_6 = 662 \mu m$, $I_{d6} = 538 \mu A$ & $I_{d4} = 393 \mu A$.

The DC gain increased to $\approx 44dB$. (2)

(1)

before;

$$g_{m5} = \mu_{ox} \frac{W}{L} (V_{GS} - V_T)^2 = 472 \mu S$$

$$g_{m1} = 47.2 \mu S$$

$$g_{ds5} = 1/r_{ds5} = 38.61 \mu$$

$$g_{ds6} = 1/r_{ds6} = \frac{662 \mu m}{130 \mu} = 5.09 \mu$$

$$g_{ds1} = 1/r_{ds1} = 2.71 \mu$$

$$g_{ds2} = 1/r_{ds2} = 0.44 \mu$$

$$R_{o2} = \frac{1}{g_{ds5} + g_{ds6}}$$

$$R_{o1} = \frac{1}{g_{ds2} + g_{ds1}}$$

$$\therefore \text{gain DC} = 47.2 \times 472 \times \frac{1}{168.61} \times \frac{1}{2.71 + 0.44} \approx 41 \Rightarrow 20 \log(41) = \underline{\underline{32dB}}$$

(2)

expected now

$$g_{ds5} = 386 \mu S$$

$$g_{ds6} = 30 \mu S$$

$$g_{ds1} = 2.71 \mu$$

$$g_{ds2} = 0.44 \mu$$

$$\Rightarrow R_{o2} = 2.4 k\Omega$$

$$\therefore \text{DC gain} = 47.2 \times 4720 \times \frac{1}{416} \times \frac{1}{3.15} = 170 \Rightarrow 20 \log(170) = \underline{\underline{44dB}}$$

It remains to determine C to satisfy bandwidth & P.M constraint.

$$5MHz = \frac{\omega_u}{2\pi} = \frac{1}{2\pi} \times \frac{47.2 \mu}{2C} \Rightarrow C = \frac{1.5 pF}{2} = \frac{C_{max}}{2} = 0.75 pF$$

$$\therefore 5MHz = \frac{\omega_u}{2\pi} = \frac{1}{2\pi} \times \frac{47.2 \mu}{2C} \Rightarrow C = 0.75 pF = C_{max}$$

Assuming that poles are far apart;

$$i.e. C_c \gg C_1$$

$$[C_c \text{ cannot be } \gg C_c \because C_{max} = 0.75p)$$

$$P.M. = \phi_M = 180^\circ + \angle AP = 180^\circ - \tan^{-1}\left(\frac{\omega_c}{P_1}\right) - \tan^{-1}\left(\frac{\omega_c}{P_2}\right) - \tan^{-1}\left(\frac{\omega_c}{\omega_z}\right)$$

$$= 180^\circ - \tan^{-1}\left(\frac{\omega_c}{\omega_{p1}}\right)$$

$$= 180^\circ - 90^\circ - \tan^{-1}\left(\frac{1}{20}\right) - \tan^{-1}\left(\frac{1}{200}\right)$$

$$= 86.85^\circ$$

But we want PM to be within 60° to 80° .

\therefore we must decrease ~~the~~ C

$$\text{for } C = 0.05 \text{ pF;}$$

$$\omega_{p2} \approx 20 \text{ MHz} \times 2\pi \quad (\text{simulation})$$

$$\omega_{p1} \text{ (reduced)} = 83.2 \text{ kHz} \times 2\pi = 2\pi \left(\frac{47.2}{4720 \times 0.05} \times 416 \right) \text{ rad/s}$$

$$\therefore \angle AP = 104.3^\circ \Rightarrow \phi_M = 75.7^\circ$$


MOSFET	gm calculated	Vgs-Vt calculated	Id calculated	gm simulated	Vgs-Vt	Id	gds
M0	150.6 μ A	0.15V	8 μ A	205 μ S	0.1431V	10.2 μ A	74.65 μ S
M1	47.22 μ S	0.257V	4 μ A	48.7 μ S	0.426V	5.063 μ A	2.74 μ S
M2	47.22 μ S	0.257V	4 μ A	48.7 μ S	0.425V	5.06 μ A	2.74 μ S
M3	47.22 μ S	0.17V	4 μ A	50.9 μ S	0.1708V	5.063 μ A	0.391 μ S
M4	47.22 μ S	0.17V	4 μ A	50.9 μ S	0.1706V	5.06 μ A	0.391 μ S
M5	4722. μ S	0.17V	401 μ A	4.49mS	0.1706	393 μ A	0.386mS
M6	9.3mS	0.15V	545 μ A	7.57mS	0.1432V	538 μ A	0.038mS

b) The Two resistors for $K=2$, $R= 500k \gg r_{ds5} || r_{ds6}$

c) DC gain = 45 db

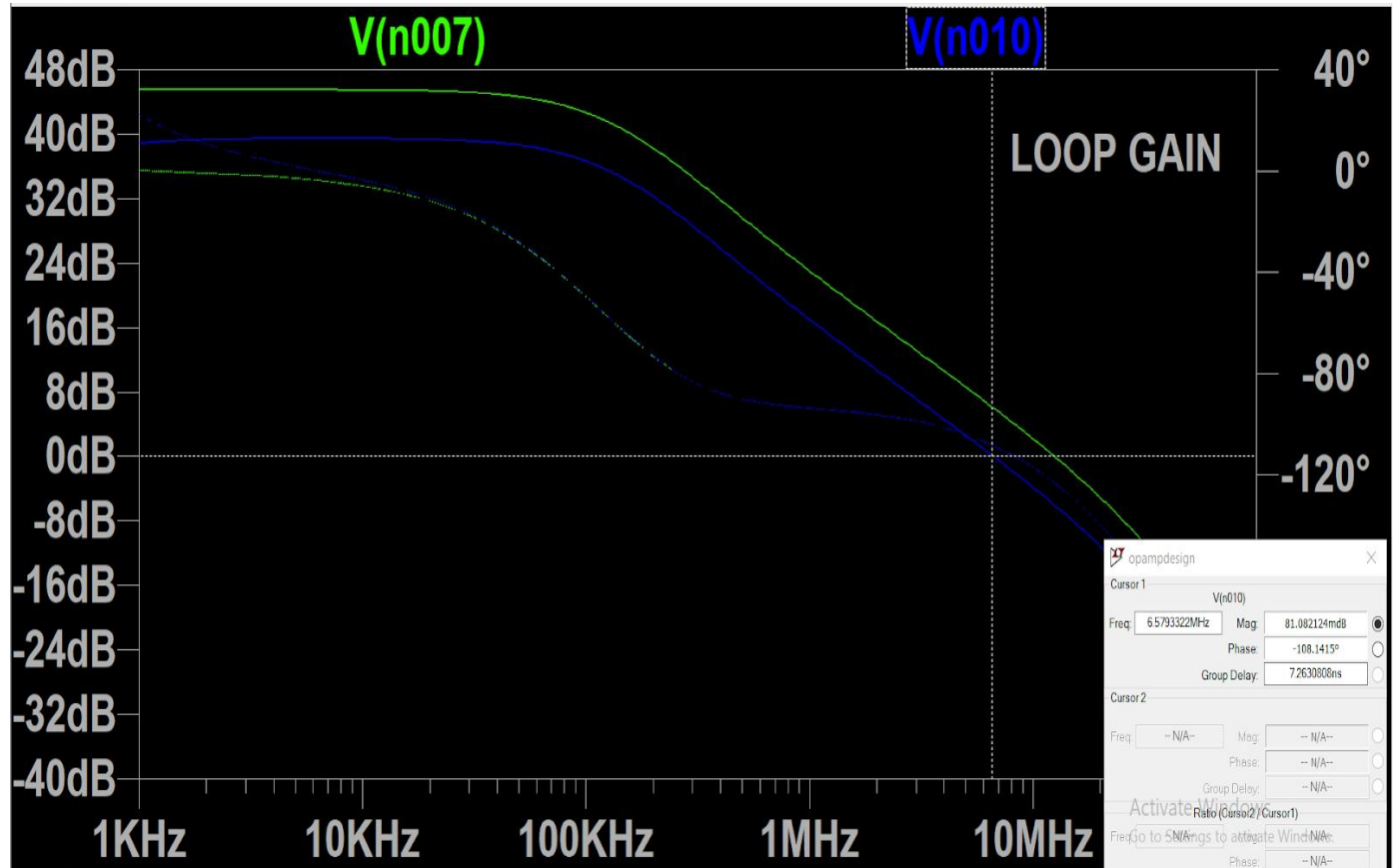d) Power consumption = 986.2 μ W

Loop Gain: Green curve opamp gain . Blue curve loop gain $=A\beta$





Phase margin=71.8 degrees

Closed Loop gain:

DC gain=5.921db

Bandwidth=6.09MHz

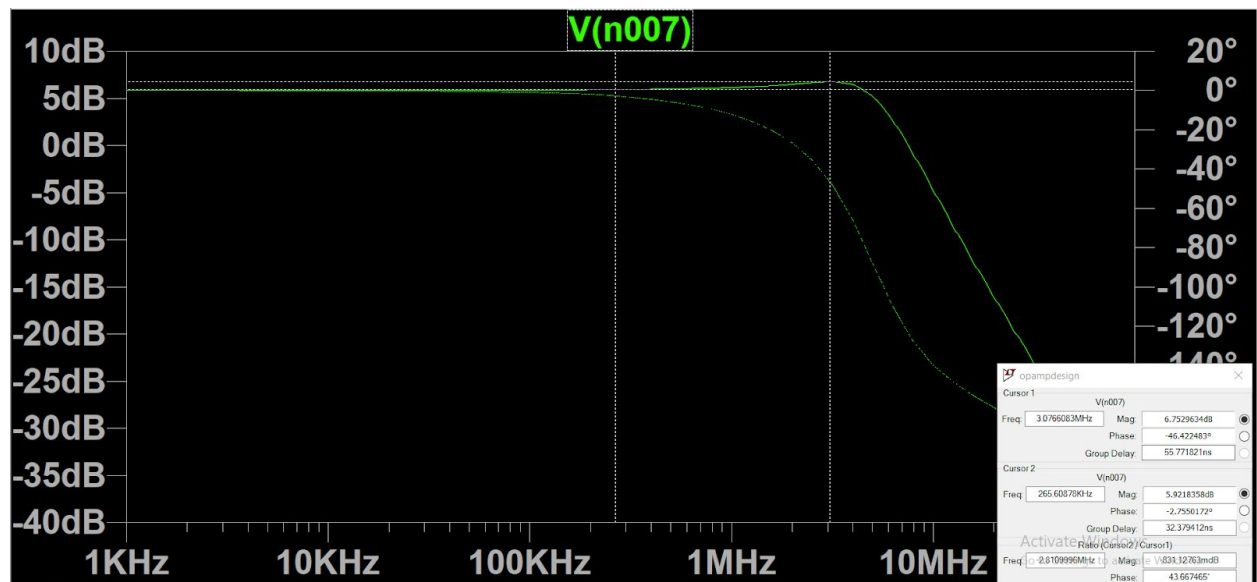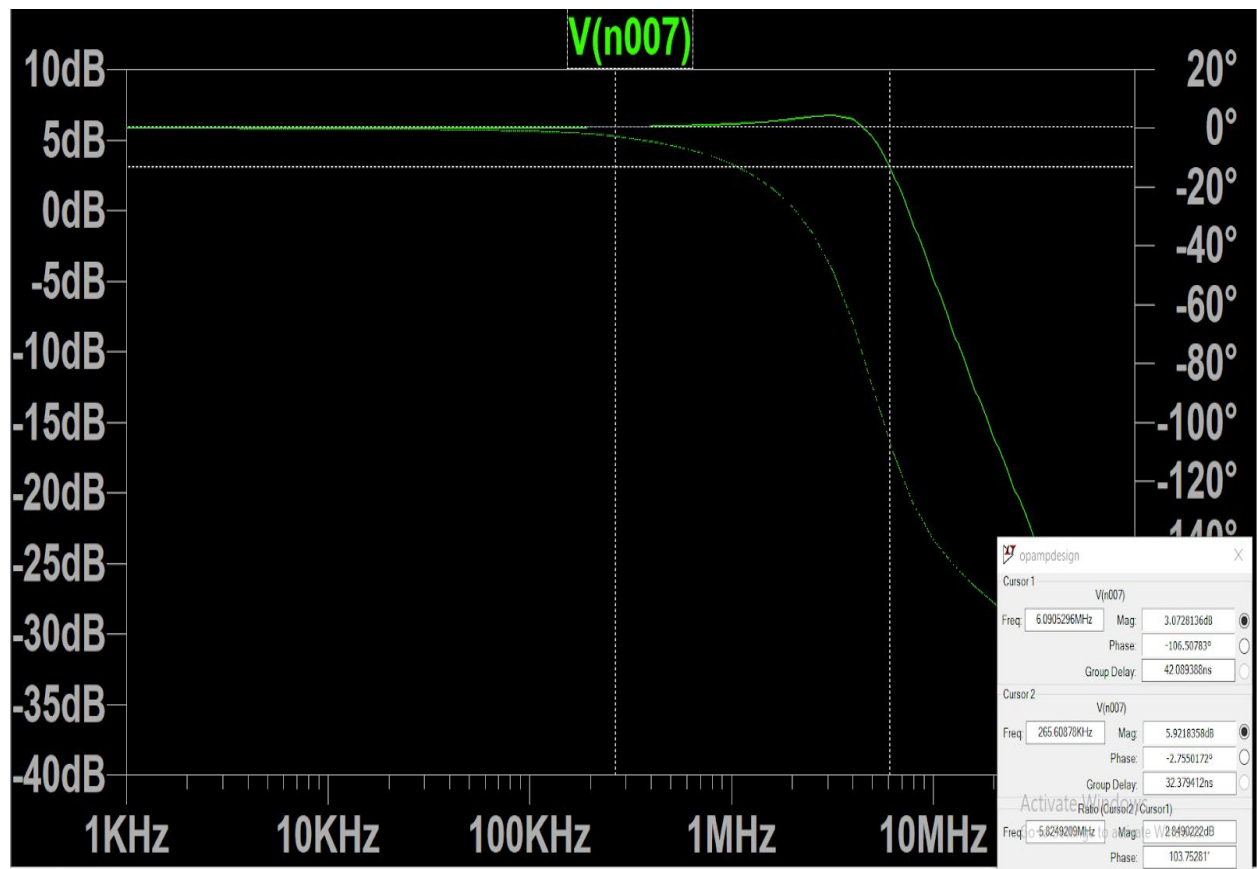


Peaking = 0.837dB

Transient Response:

Blue curve : input step

Green curve: output response

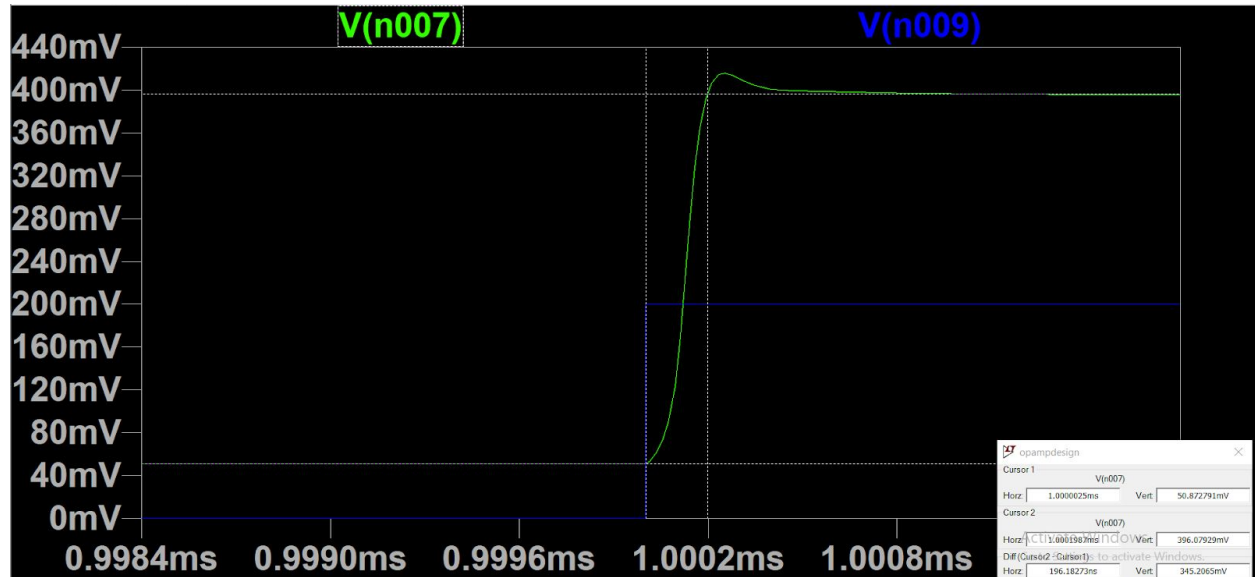

$t_{rise} = 196.2 \text{ ns}$

$\% \text{Overshoot} = 4.85\%$

$t_s = 314 \text{ ns}$

FINAL DESIGN:

Designed $C = 0.05 \text{ pf}$

$V_{CM} = 180 \text{ mV}$

$i_0 = 1.11 \mu\text{A}$

MOSFET	W	L	W/L
M00	1.8u	1.8u	1
M0	18u	1.8u	10
M1	9u	1.8u	5
M2	9u	1.8u	5
M3	3.91u	1.8u	2.174
M4	3.91u	1.8u	2.174
M5	217.4u	1.8u	120.78
M6	662u	1.0u	662